

Executive Summary

- Motivation: We need a working ALU for the microprocessor design.
- Problem: We need to put together and test the building blocks for the microprocessor design.
- Overview:
 - ALU implementation and testing.
 - Introduce Project Logistics.
- Conclusion: We can implement an ALU using logic building blocks, and we can evaluate its design. We are ready to work in our microprocessor!



ALU Implementation

Course Logistics



ALU Implementation


Course Logistics



Recall: Arithmetic Logic Unit

- ALU is the heart of the processor.
- ALU should perform at least:
 - Addition
 - Subtraction
 - AND
 - OR


ALUControl _{1:0}	Function
00	Add
01	Subtract
10	AND
11	OR

 

Example: Perform A + B ALUControl = 00 Result = A + B



Inputs and Outputs

 


ALU OR

ALUControl _{1:0}	Function
00	Add
01	Subtract
10	AND
11	OR

Example: Perform A OR B

 $ALUControl_{1:0} = 11$ Mux selects output of OR gate as *Result*, so

Result = A OR B

 




ALU ADD

ALUControl _{1:0}	Function
00	Add
01	Subtract
10	AND
11	OR

 Example: Perform A + B

 $ALUControl_{1:0} = 00$ $ALUControl_0 = 0$, so: Cin to adder = 0 2^{nd} input to adder is B Mux selects Sum as Result, so Result = A + B






Operation Logic

```
assign condinvb = ALUControl[0] ? ~b : b;
assign sum = a + condinvb + ALUControl[0];


always @(*)
begin
   casex (ALUControl[1:0])
    2'b0?: Result = sum;
   2'b10: Result = a & b;
   2'b11: Result = a | b;
   endcase
end
```

 




ALU with Status Flags

Flag	Description
N	Result is Negative
Z	Result is Zero
С	Adder produces Carry
	out
V	Adder o <mark>V</mark> erflowed

 




ALU with Status Flags

 



Flag Negative (N)

 


N = 1 if:

Result is negative

So, N is connected to most significant bit (msb) of Result



Flag Zero (Z)

 

```
Z = 1 if:
all of the bits of
Result are 0
```


```
E.g.: Result = 0101

~Result = 1010

Z=AND(Result bits) = 0
```



Flag Carry (C)

 

C = 1 if:


C_{out} of Adder is 1

AND

ALU is adding or subtracting (ALUControl is 00 or 01)



Flag Overflow (V)

 


V = 1 if:

The addition of 2 samesigned numbers produces a result with the opposite sign



Flag Overflow (V)

 

$$V = 1$$
 if:

ALU is performing addition or subtraction $(ALUControl_1 = 0)$

AND

A and Sum have opposite signs

AND


{ A and B have same signs upon addition $(ALUControl_0 = 0)$

OR

A and B have different signs upon subtraction $(ALUControl_0 = 1)$



Flags Assignment

 

Outline

ALU Implementation

Course Logistics



Arch Project

- Define teamworks for the final Project.
 - Up to 3 members.
- Collaboration also for: Laboratory 04, 05 and 06.
- Final project details will be revealed during next week.

For starting:

- Recall: Verilog and ASM.
- Recall: Topics from ISA to Microarchitecture.
- Recall: Floating Point Arithmetic from Discrete Structures II.
- First job: complete Lab 04 (next lab)



Outline

ALU Implementation

Course Logistics



- We implemented an ALU that can be used as building blocks for our microprocessor.
- We evaluated the ALU using the testvector testbench.
- We conclude that the ALU enables our microprocessor design.



Computer Architecture



CS3501 - 2023I

PROF.: JGONZALEZ@UTEC.EDU.PE

